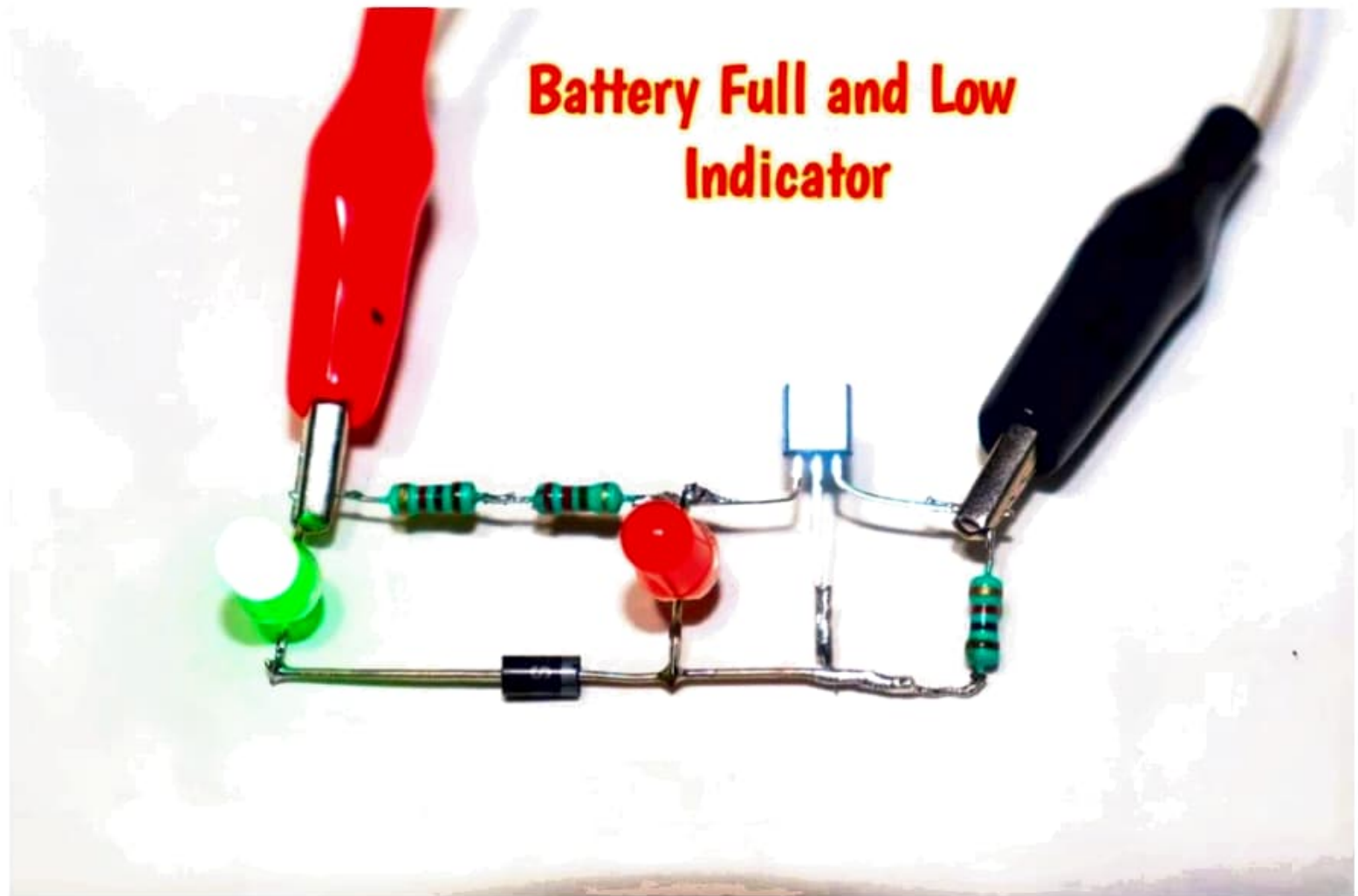


3.7V Battery Low and Full Level Indicator Circuit

Introduction: 3.7V Battery Low and Full Level Indicator Circuit




Hii friend,

Today I am going to make a circuit of 3.7V Battery low and full charge indicator.

Let's get started,

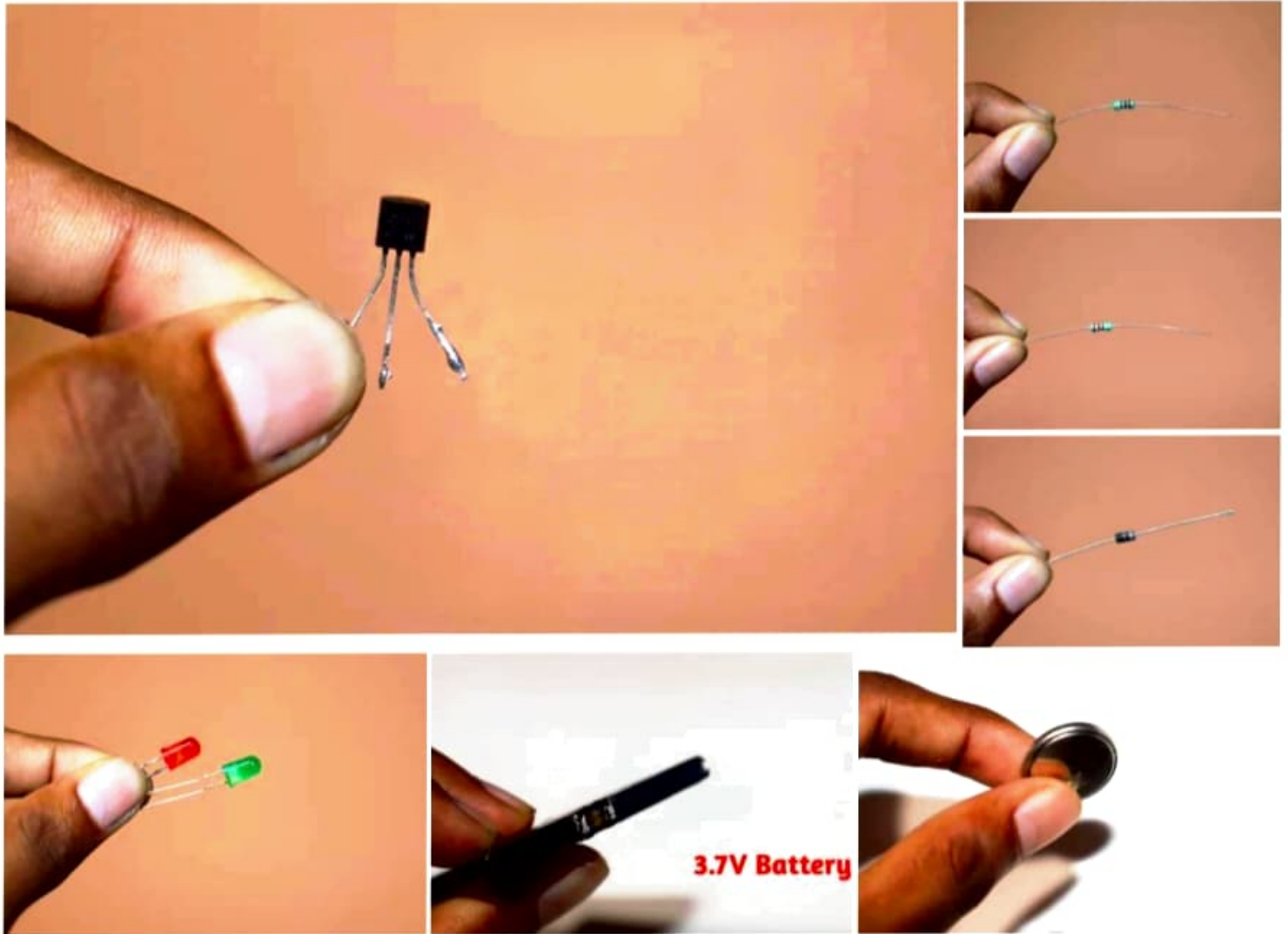Step 1: Take All Components As Shown Below



Components required -

- (1.) Transistor - **BC547** x1
- (2.) Resistor - **1K** x2
- (3.) Resistor - **220 ohm** x3
- (4.) pn-Junction Diode - **1N4007** x1
- (5.) LED - **3V** x2 (Red for Low charge indication and Green for Full charge indication)
- (6.) Battery - 3.7V and 3V

Step 2: Connect 1k Resistor



Firstly we have to connect 1K resistor to Base and emitter pin of the transistor as solder in the picture.

Step 3: Connect 220 Ohm Resistor



Next solder 220 ohm resistor to collector pin of the transistor as you can see in the picture.


Step 4: Connect 1K Resistor Again



Next we have to connect 1K resistor again.

Solder 1K resistor in series to 220 ohm resistor as solder in the picture.


Step 5: Connect 1N4007 Diode

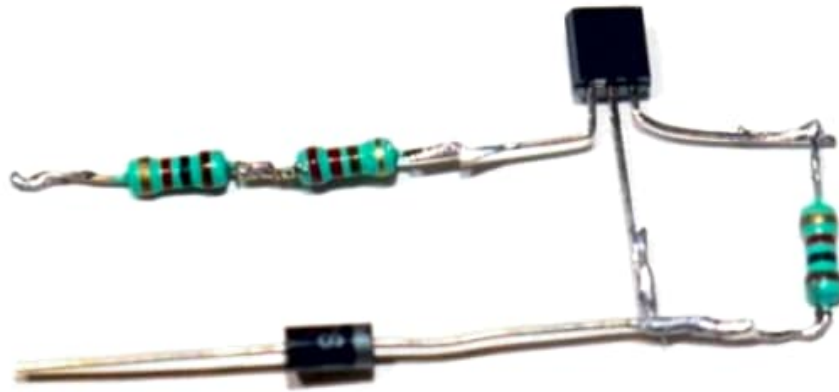

Next connect 1N4007 Diode to the circuit.


Solder -ve of Diode to base pin of Transistor as picture.

Step 6: Connect Green LED

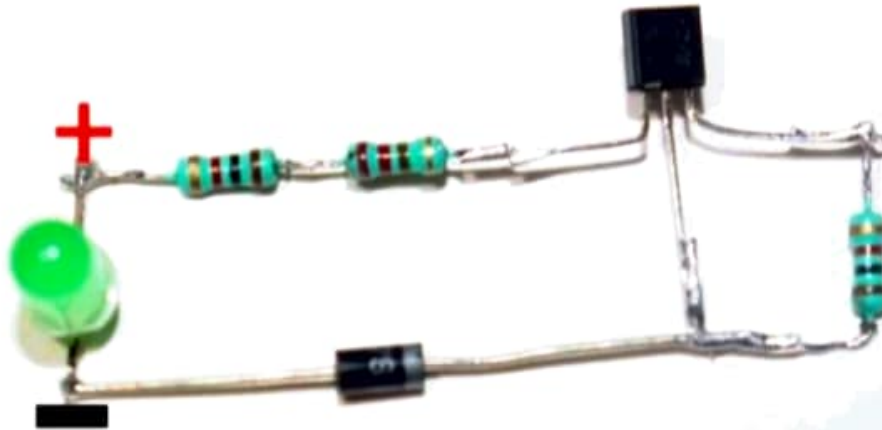


Next Solder +ve leg of green LED to 1K resistor which is connected to collector pin of transistor and solder -ve pin of green LED to +ve of diode as you can see in the picture.

Step 7: Connect Red LED

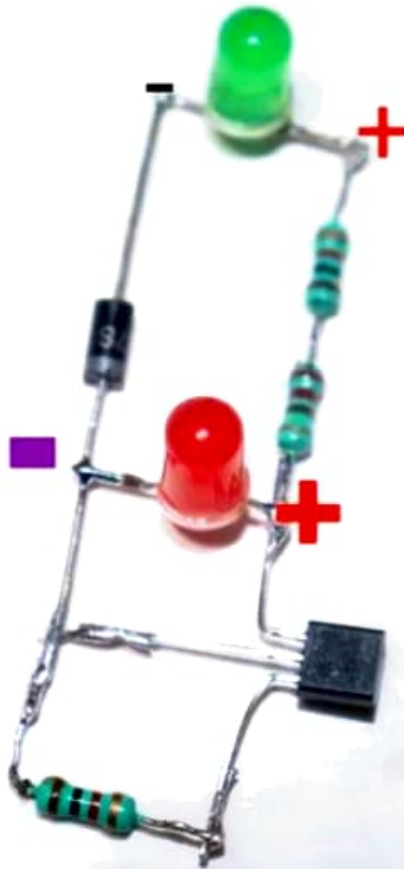

Next Solder +ve leg of Red LED to Collector of transistor and solder -ve leg of Red LED to -ve of diode as solder in the picture.

Step 8: Testing - 1

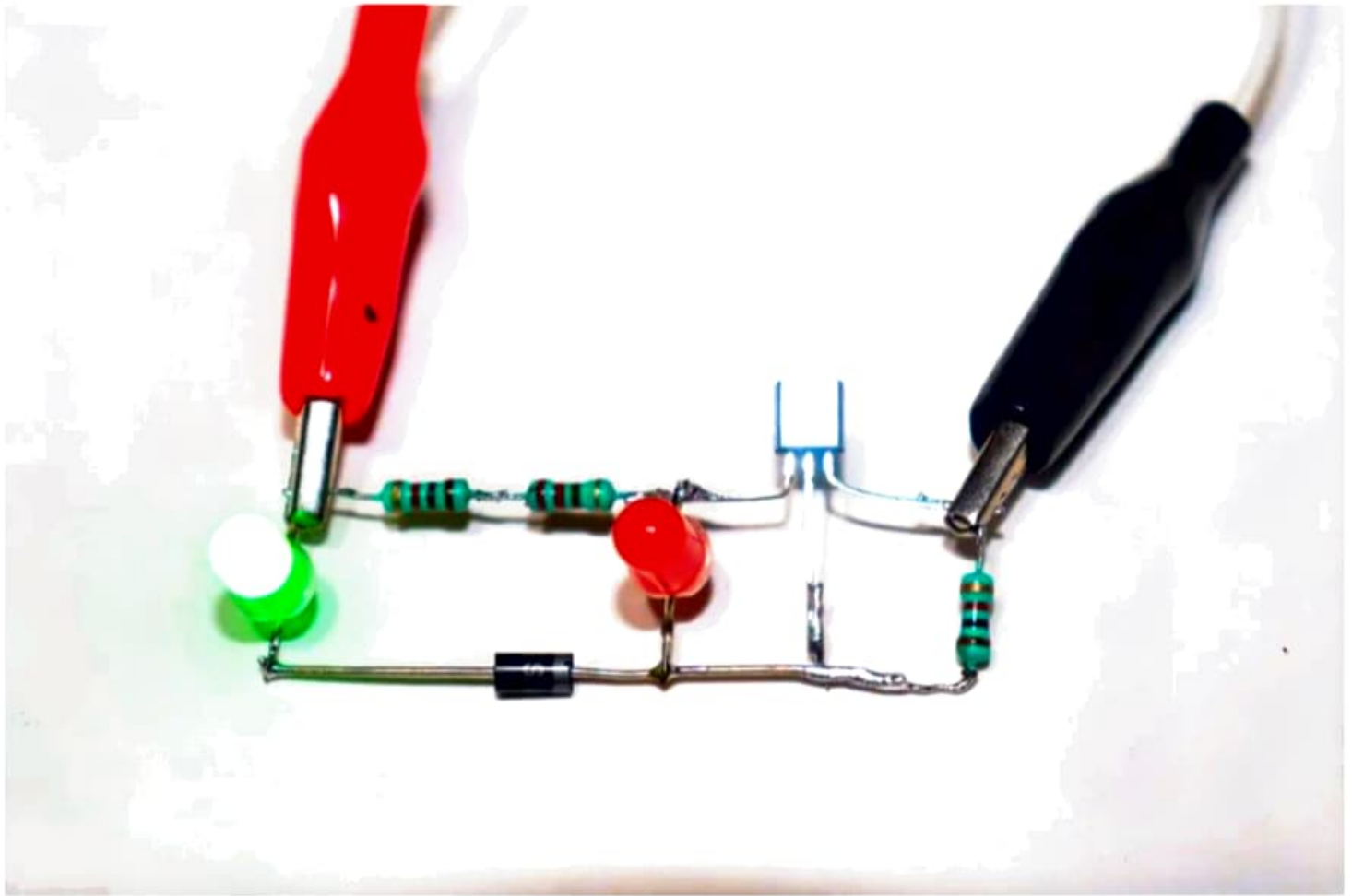


Now our circuit is completed and now we have to check this circuit.

Connect +ve of 3V battery to +ve leg of green LED and -ve of 3V battery to emitter pin of the transistor or as you can see in the picture.

~ As in above picture glowing Green LED Because this battery is fully charged.

Step 9: Testing - 2

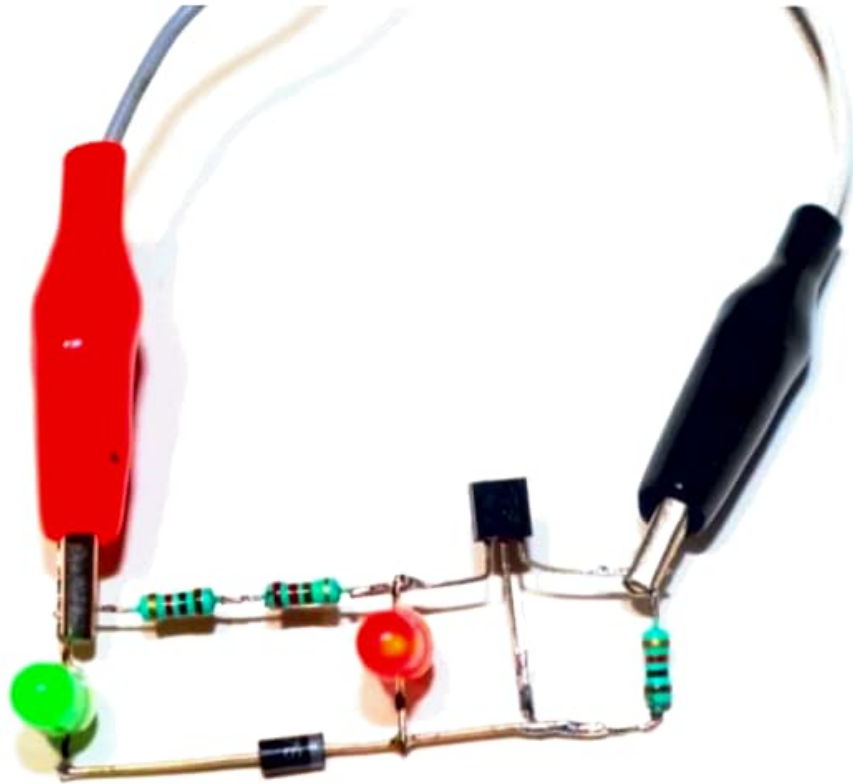

When I connected 3V battery then Red LED is glowing and Green LED is also glowing in small amount.

~ Hence when Battery will be full charge i.e. 3.7V then Green LED will glow only and when battery will be low i.e. 1.5V then Red LED will glow only.

Thank you